

Low Power Design


NCTU-EE ICLab Spring 2022



Lecturer : Yu Lun, Hsu

Why Low Power?

 - **Power \uparrow \rightarrow Temperature \uparrow \rightarrow Safety \downarrow**
- **May lead to permanent damage to the chip**
- **Portable device require low power**



Outline

■ Power Dissipation

- Static Power Dissipation
- Dynamic Power Dissipation

■ Low Power Design Introduction

■ Static Power Reduction

- Multi Threshold Voltage

■ Dynamic Power Reduction

- Multi Voltage
- Power Gating
- RTL and Architecture Design Techniques
- Clock gating

■ Reference



Outline

■ Power Dissipation

- Static Power Dissipation
- Dynamic Power Dissipation

■ Low Power Design Introduction

■ Static Power Reduction

- Multi Threshold Voltage

■ Dynamic Power Reduction

- Multi Voltage
- Power Gating
- RTL and Architecture Design Techniques
- Clock gating

■ Reference



Power Dissipation


➤ $P_{\text{total}} = P_{\text{static}} + P_{\text{dynamic}}$

➤ **Static power (P_{static})**

- $P_{\text{static}} = I_{\text{leakage}} * V_{\text{dd}}$
 - I_{leakage} : leakage current

➤ **Dynamic power (dominated)**

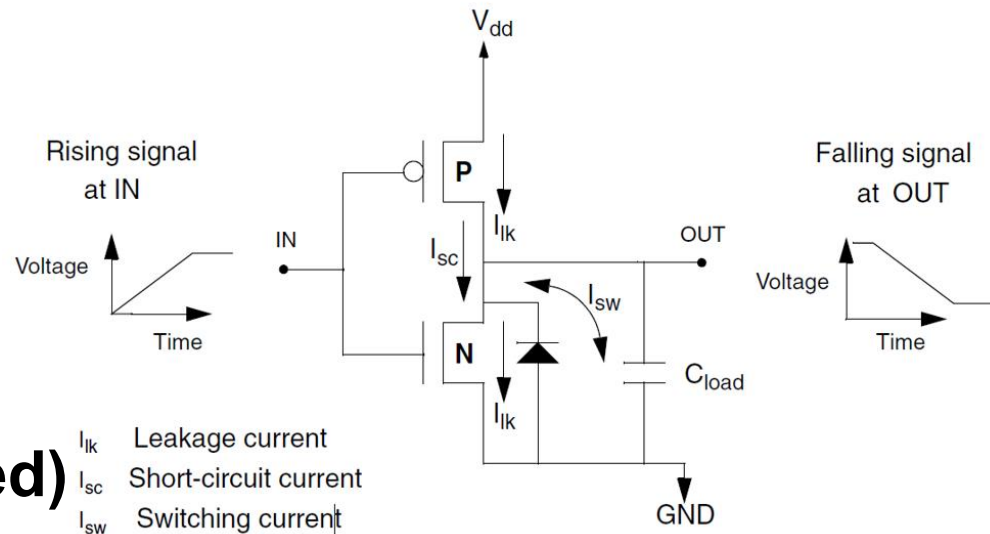
- $P_{\text{dynamic}} = p_t * (P_{\text{sw}} + P_{\text{sc}})$
 - p_t : Switching Probability of one clock cycle
- **Switching power (P_{sw})**
 - Charging and discharging parasitic capacitance
- **Short circuit power (P_{sc})**
 - Direct path between V_{dd} and GND when switching



Static Power Dissipation

➤ Caused by leakage current

 - **Sub-threshold current**
 - Dominate the leakage current
 - Increase with temperature
- **Reverse leakage current**
 - Happen when device is reverse biased
 - Increase with temperature
- **Gate Leakage current**
 - Increase with V_{dd}



I1-Reverse Bias p-n Junction Leakage
I2-Sub Threshold/ Weak Inversion Current
I3-Gate Leakage, Tunneling Current through Oxide
I4-Gate Current due to hot carrier Injection
I5-Gate Induced Drain Leakage(GIDL)



➤ How to minimize static power?

- Reduce voltage supply (**Process dependent**)
- In general: the leakage current can't be changed if process and cells are decided

Dynamic Power Dissipation

➤ $P_{\text{dynamic}} = p_t * (P_{\text{sw}} + P_{\text{sc}})$

  - **pt : Switching Probability**
- **$P_{\text{sw}} = C_L * V_{\text{dd}}^2 * f_p$**
 - Charge and discharge the loading capacitive
- **Psc: Short circuit power**
 - Both NMOS and PMOS are turned on



➤ **How to minimize dynamic power?**

- Reduce V_{dd} (*process dependent*) → P_{sw} & P_{sc}
- Reduce parasitic capacitance → P_{sw}
- Reduce the overlap time of PMOS and NMOS turn-on time, i.e., keep the input signal rise/fall time the same → P_{sc}
- Reduce unnecessary switching activities → P_t
 - Gated clock (Turn off unused circuits)
 - Register retiming




Outline

- Power Dissipation
 - Static Power Dissipation
 - Dynamic Power Dissipation
- **Low Power Design Introduction**
- Static Power Reduction
 - Multi Threshold Voltage
- Dynamic Power Reduction
 - Multi Voltage
 - Power Gating
 - RTL and Architecture Design Techniques
 - Clock gating
- Reference



Low Power Design Methodologies

➤ Where to reduce?

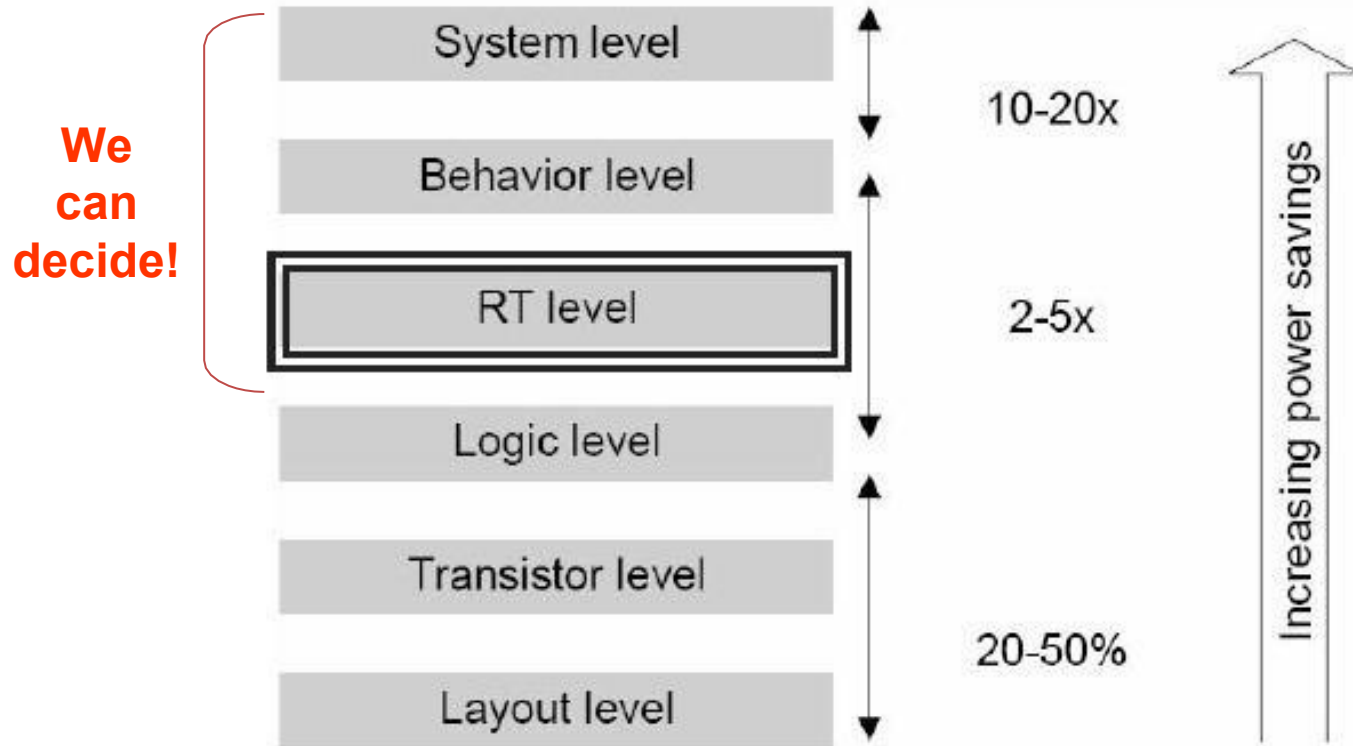

REF: H. Mizas, D. Soudris, S. Theoharis, G. Theodoridis, A. Thanailakis, and C.E. Goutis, "Structure of the Low-Power Design Flow, " 25/6/1998.

Outline

- Power Dissipation
 - Static Power Dissipation
 - Dynamic Power Dissipation
- Low Power Design Introduction
- **Static Power Reduction**
 - Multi Threshold Voltage
- Dynamic Power Reduction
 - Multi Voltage
 - Power Gating
 - RTL and Architecture Design Techniques
 - Clock gating
- Reference




Multi Vt

➤ Current of MOS:

$$I_{sub} = I_s \cdot e^{\frac{q(V_{GS} - V_T - V_{offset})}{nKT}} \left(1 - e^{\frac{-qV_{DS}}{KT}}\right)$$

$$P_{static} \approx I_{sub} V_{DD}$$

 

Vt ↓, I_{sub} ↑, I_{ds} ↑, speed ↑, delay ↓




Vt Scaling

➤ As V_t decrease, sub-threshold leakage increases

- approaching 10% in 0.18 μm technology
- $V_t \downarrow$, $I_{\text{DS_sub}} \uparrow$, $I_{\text{D(SAT)}} \uparrow$

 Active Power vs Vdd at Constant Frequency



The x-axis represents the supply voltage required maintain the device at a fixed frequency, while allowing the threshold voltage to vary to meet the fixed frequency specification.

Vt Scaling

- When Power is a concern : High Vt logic gate
- When Delay time is a concern : Low Vt logic gate

 


Figure 2-5 Leakage vs. Delay for a 90nm Library



Outline

- Power Dissipation
 - Static Power Dissipation
 - Dynamic Power Dissipation
- Low Power Design Introduction
- Static Power Reduction
 - Multi Threshold Voltage
- **Dynamic Power Reduction**
 - Multi Voltage
 - Power Gating
 - RTL and Architecture Design Techniques
 - Clock gating
- Reference




Multi Voltage

➤ Dynamic Power:

$$P_{dyn} = \underbrace{(C_{eff} \cdot V_{dd}^2 \cdot f_{clock})}_{\text{Switching power}} + \underbrace{(t_{sc} \cdot V_{dd} \cdot I_{peak} \cdot f_{clock})}_{\text{Short circuit power}}$$

 
- Reducing the Vdd is the most straight forward way to reduce the power.
- However, decreasing Vdd would cause the circuit delay increasing.



*CMOS example



Multi Voltage example

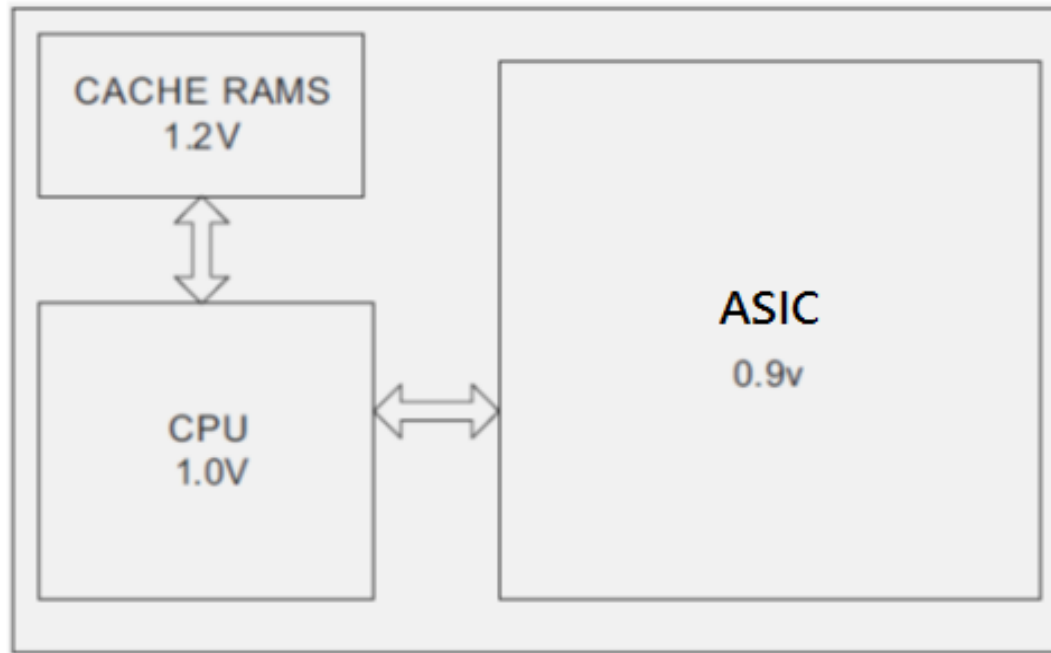

- The cache RAMS are run at the highest voltage because they are on the critical timing path.
- The CPU is run at a high voltage because its performance determines system performance.
- The rest of the chip can run at a lower voltage still without impacting overall system performance.



Multi Voltage Strategies

➤ **Static Voltage Scaling (SVS):**

- Different blocks or subsystems are given different, fixed supply voltages.

➤ **Multi-level Voltage Scaling (MVS):**

- A block or subsystem is switched between two or more voltage levels.
- Only a few, fixed, discrete levels are supported for different operating modes.


➤ **Dynamic Voltage and Frequency Scaling (DVFS):**

- An extension of MVS where a larger number of voltage levels are dynamically switched to follow changing workloads.



Multi Voltage Strategies

 - **Dynamic Voltage and Frequency Scaling (DVFS):**
 - **Compute bound in DVFS**
 - Chips can only work at the region below compute bound.
 - DVFS must adjust vdd first before raising frequency, and drop frequency first before turning down vdd.





Level Shifter

➤ Connecting 2 power domains at different voltage levels can cause design issues


- Timing inaccuracy
- Signals are not propagated

➤ A level shifter is required ⇒ 利用 level shifter 加減圧


- High to low
- Low to High

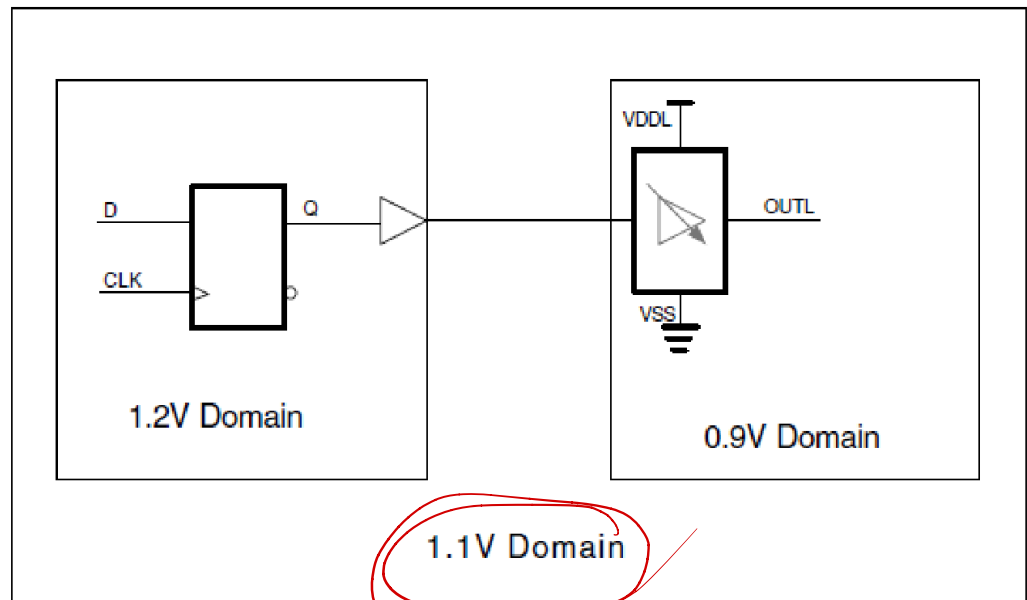 


Level Shifter

 


Level Shifter

 


Level Shifter

 


Level Shifter

 


Level Shifter

 


Level Shifter

 


Level Shifter

 

Level Shifter

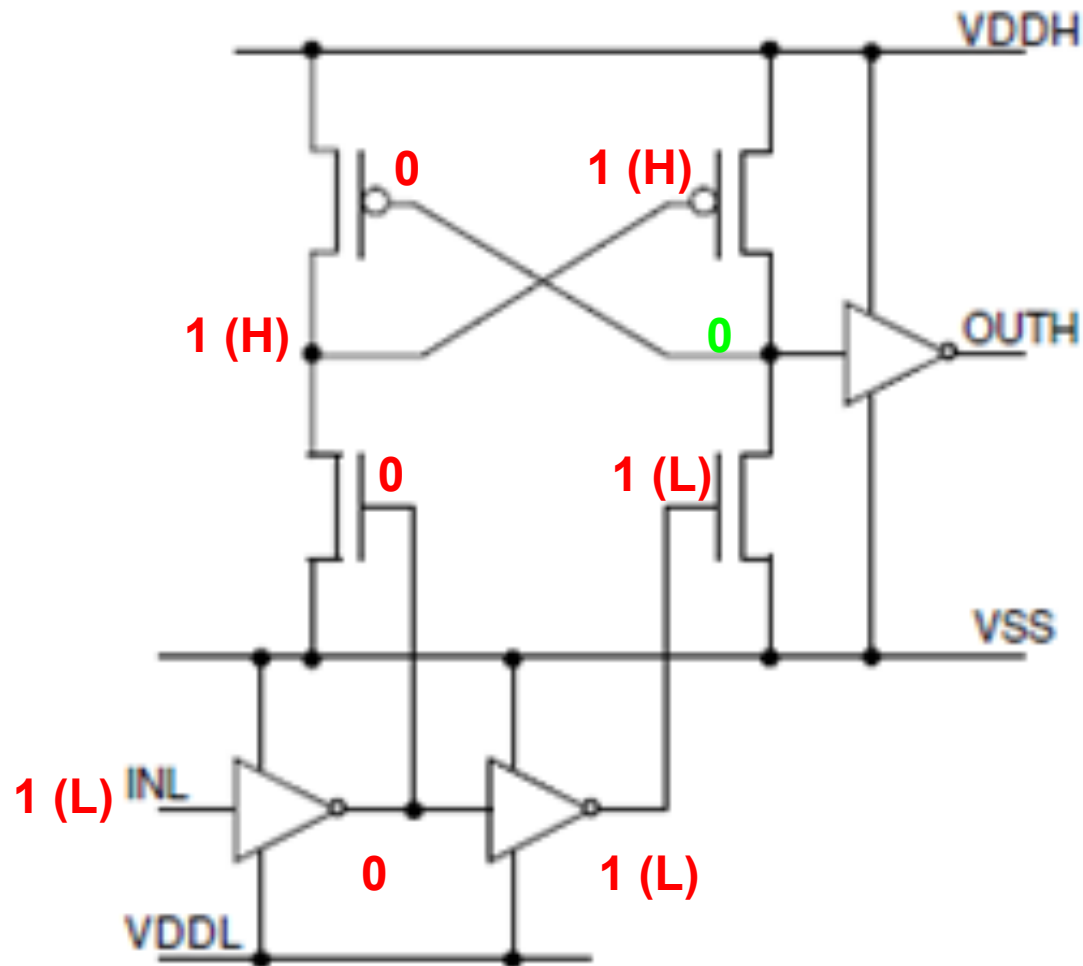

Level Shifter

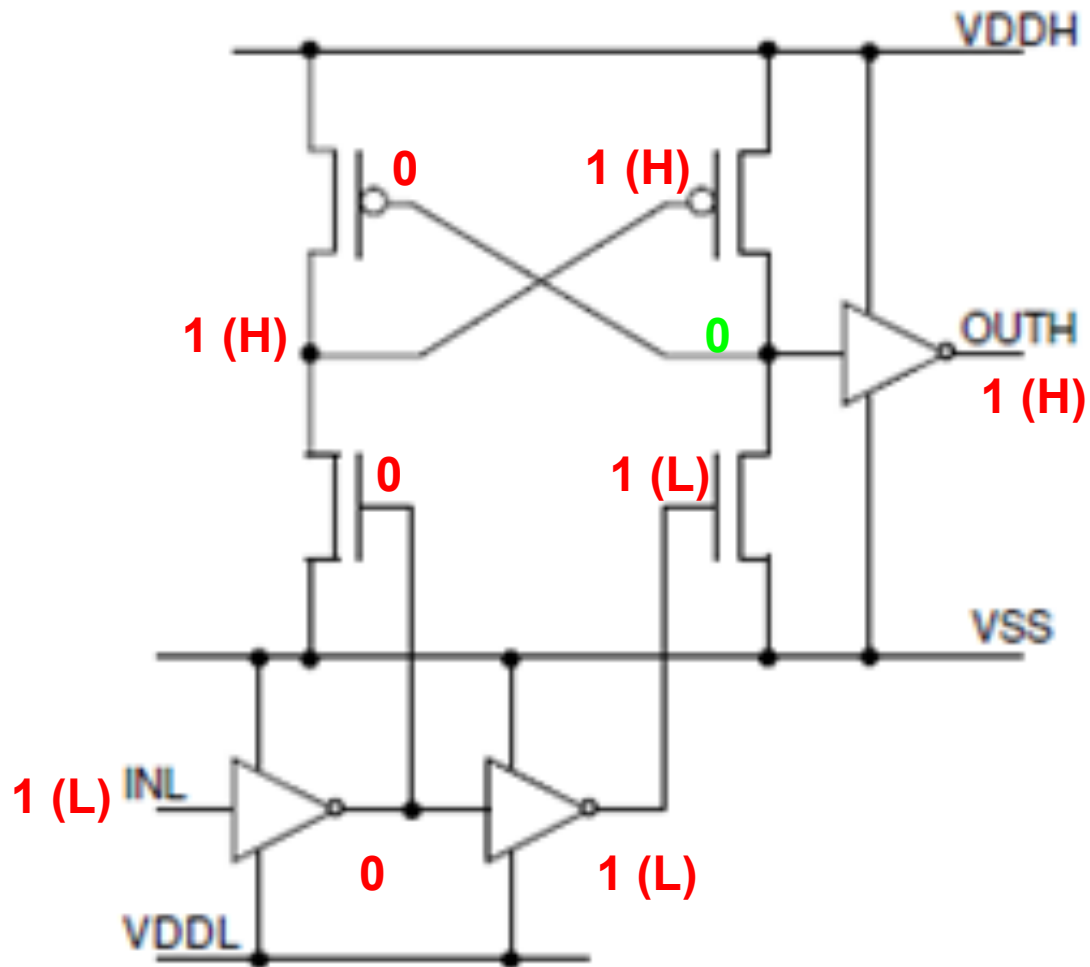

Outline

- Power Dissipation
 - Static Power Dissipation
 - Dynamic Power Dissipation
- Low Power Design Introduction
- Static Power Reduction
 - Multi Threshold Voltage
- **Dynamic Power Reduction**
 - Multi Voltage
 - Power Gating
 - RTL and Architecture Design Techniques
 - Clock gating
- Reference



Power Gating

- The basic idea of power gating is to provide two power modes : A **low power mode** and an **active mode**.
- The goal is to switch between these mode to maximize power savings while minimizing the impact to performance.
- Sleep mode (low power mode) : shut down power to block of logic.

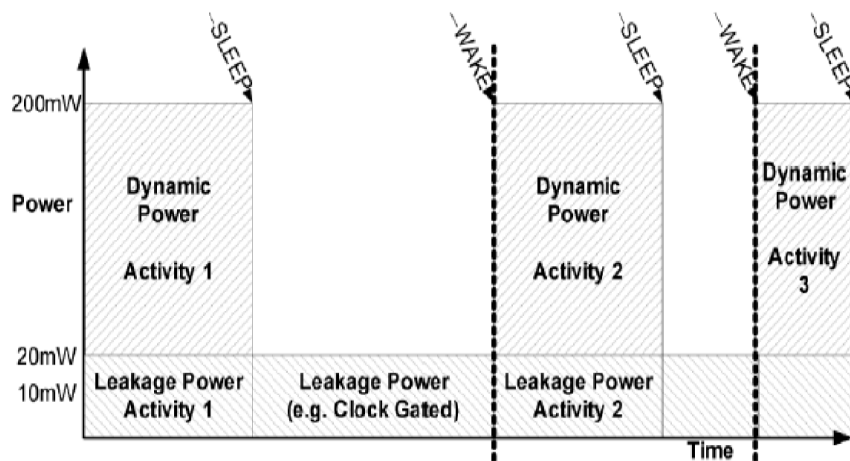


Figure 4-1 Activity Profile with No Power Gating


 



Figure 4-3 Realistic Profile with Power Gating

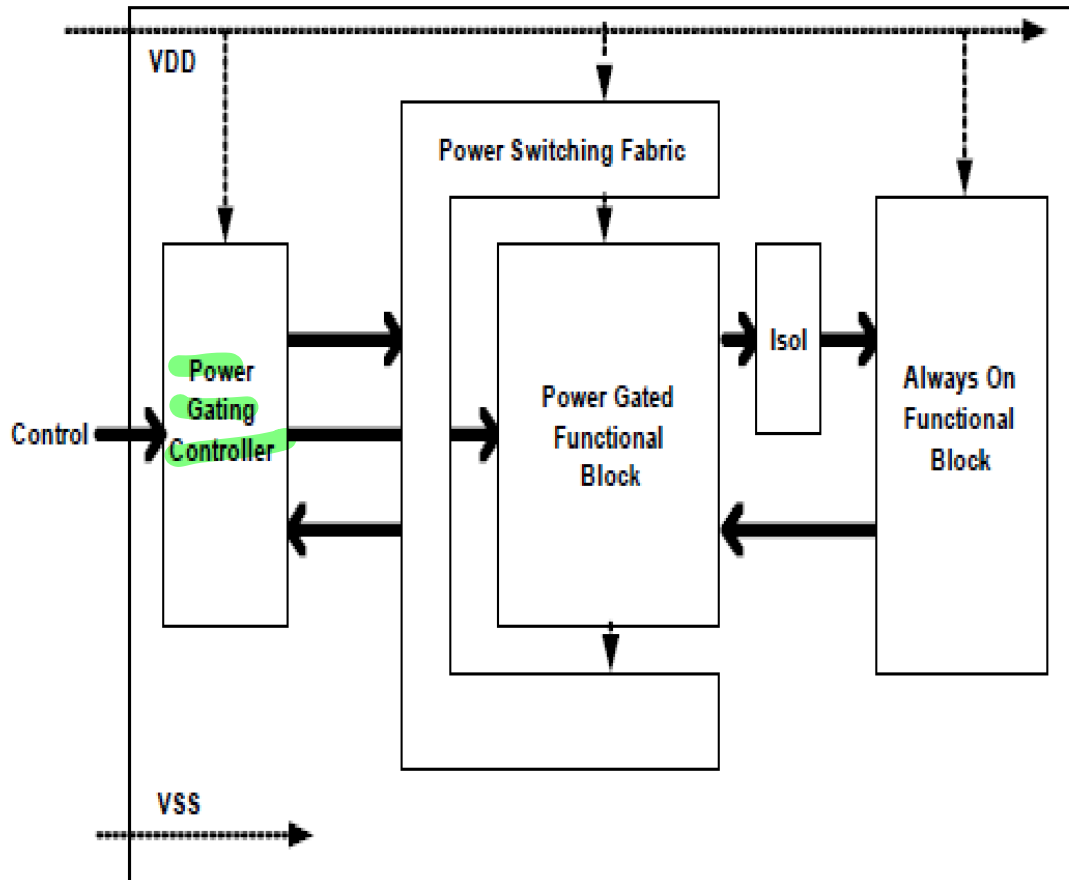


Power Gating example




Power switching fabric :

 

Isolation :

 


	0	1
0	0	0
1	0	1

 


	0	1
0	0	1
1	1	1


Power Gating example

 


Power switching fabric :

 


Isolation :

 


Power Gating example

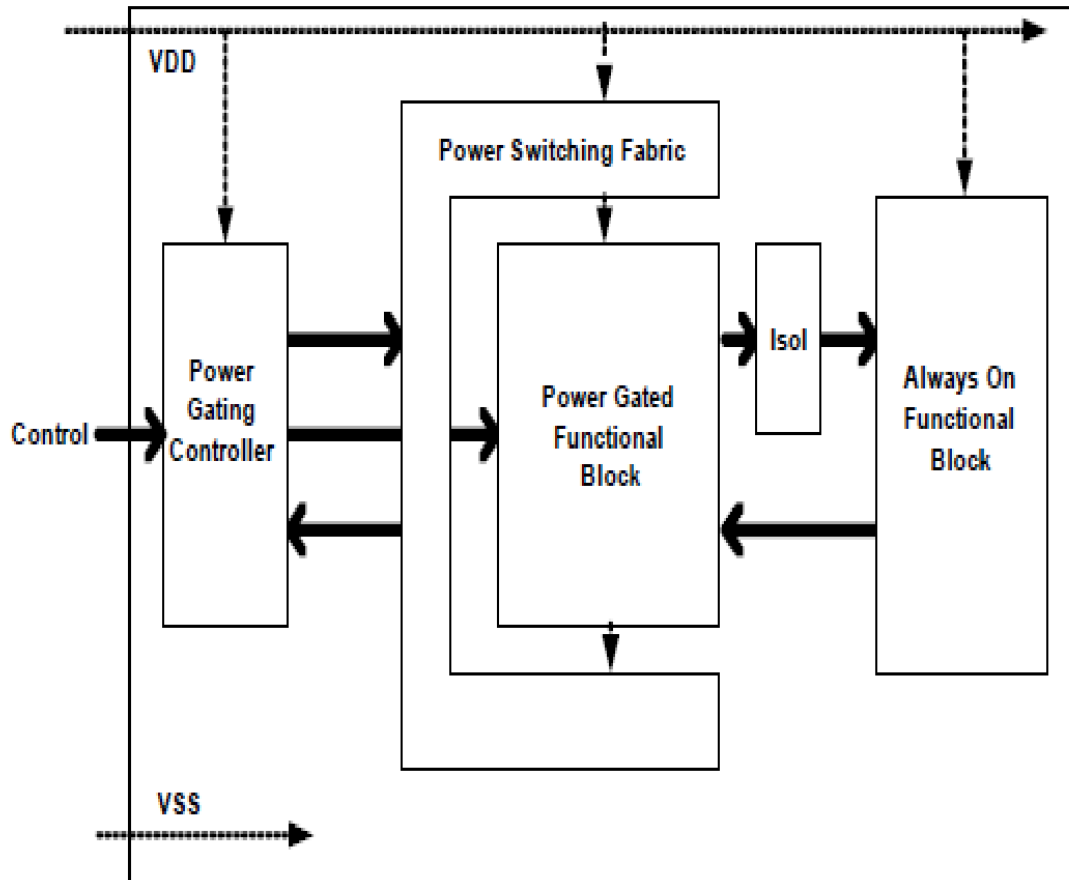


Power switching fabric :

 


Isolation :

 


Power Gating example

 


Power switching fabric :

 


Isolation :

 


Power Gating example

 

Power switching fabric :


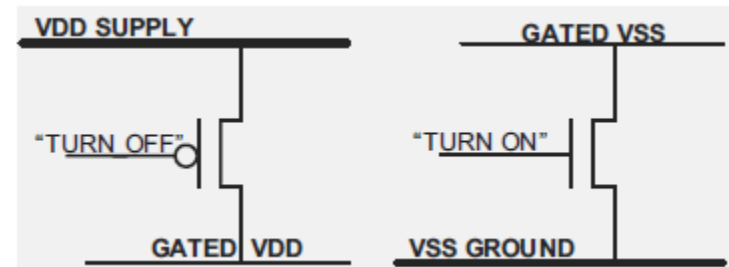


Isolation :

 


Retention registers

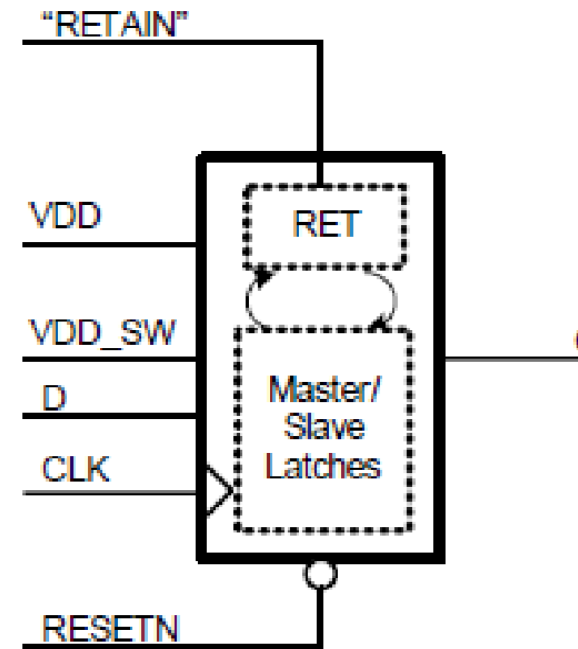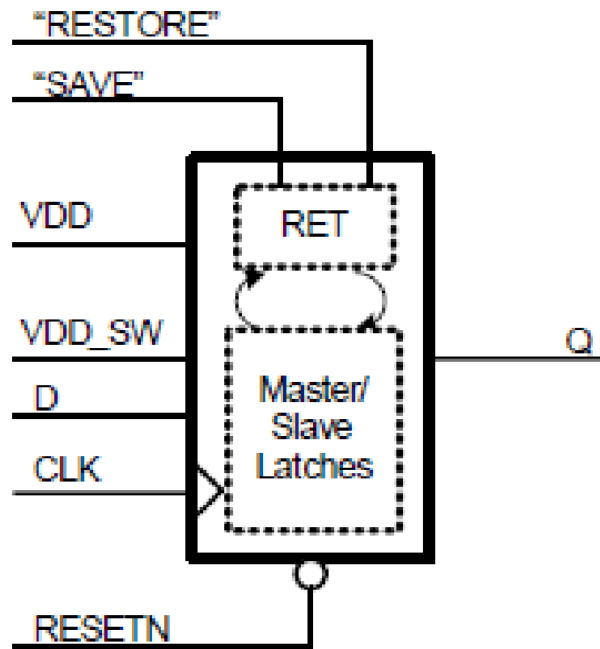- States of some registers in shut-down mode need to be preserved
- Retention registers can **store data while in shut-down mode**



Power Control Sequencing

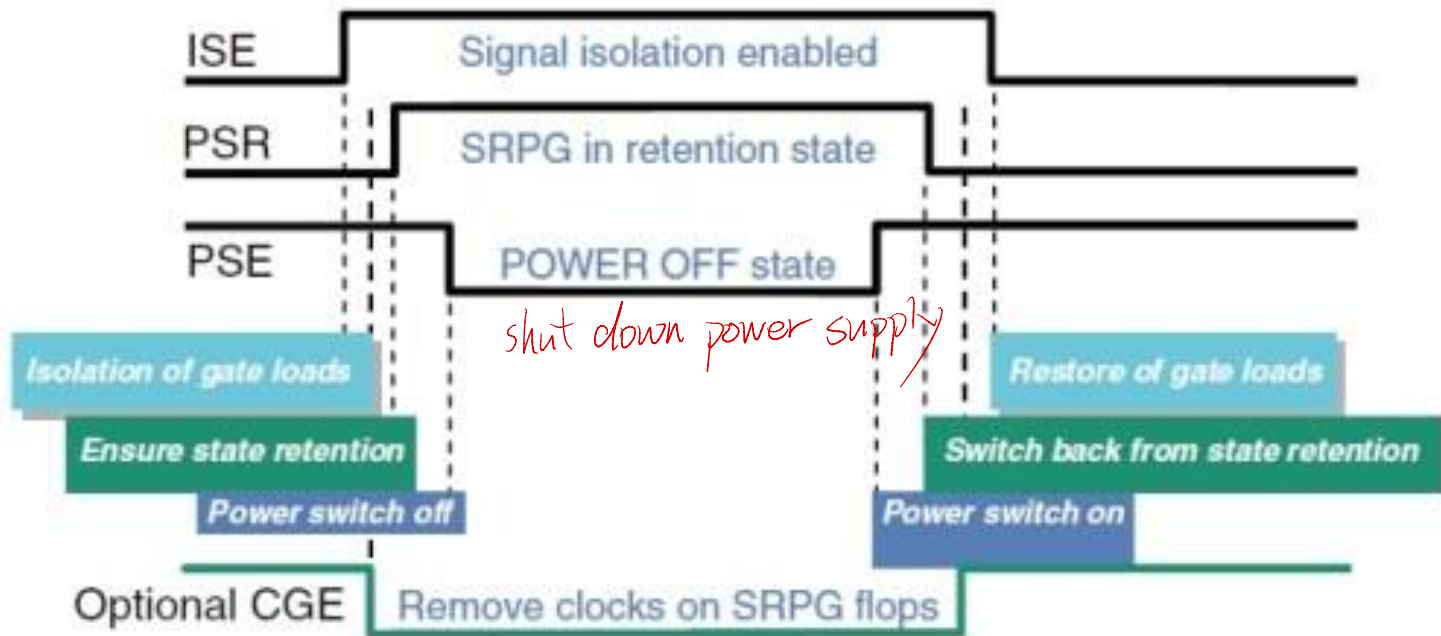- Power gating needs a control circuit to schedule the whole procedure.




*SRPG : State Retention Power Gating Cell


https://semiengineering.com/knowledge_centers/low-power/techniques/power-cycle-sequencing/

Unified Power Format(UPF)

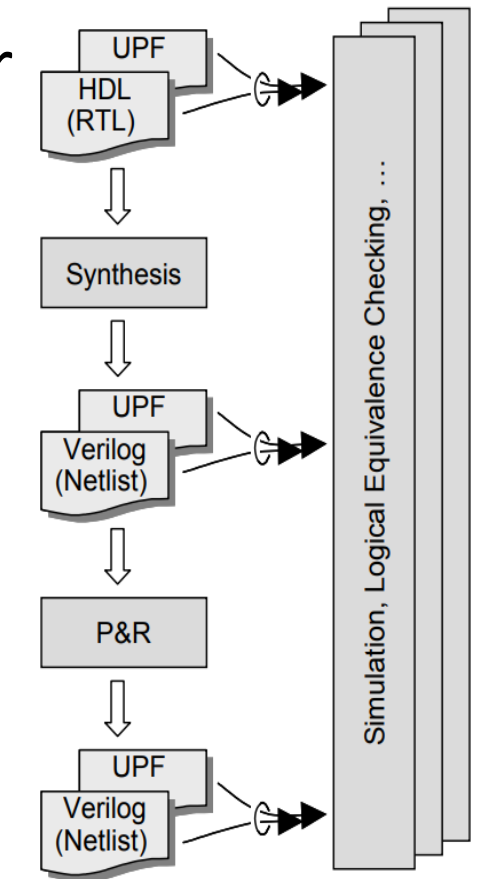- Unified Power Format : TCL-based power specification file
- UPF files consists of commands and objects that describe power intent.
- `irun -lps_1801 <upf_file>`



Unified Power Format(UPF)

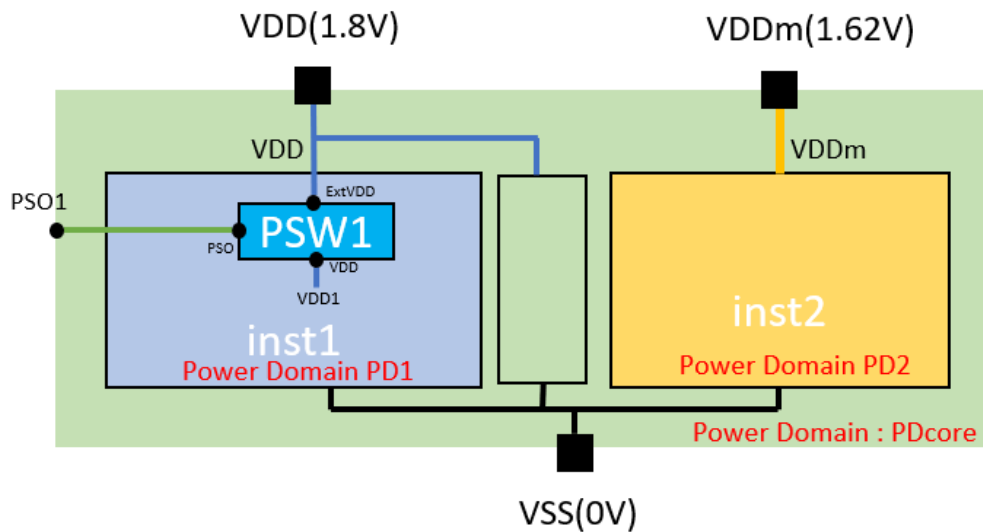

- Create supply nets & supply ports
- Create supply sets and associate power domains
- Create power switches
- Set isolation strategies
- Set level shifter strategies
- Create power state table

For more detail about UPF, please refer to [IEEE Standard for Design and Verification of Low-Power, EnergyAware Electronic Systems](#)

Outline


- Power Dissipation
 - Static Power Dissipation
 - Dynamic Power Dissipation
- Low Power Design Introduction
- Static Power Reduction
 - Multi Threshold Voltage
- **Dynamic Power Reduction**
 - Multi Voltage
 - Power Gating
 - RTL and Architecture Design Techniques
 - Clock gating
- Reference



Architecture Trade-offs: Power/Frequency/Area

- Trade off clock frequency for area to reduce power.


Consider the following reference design

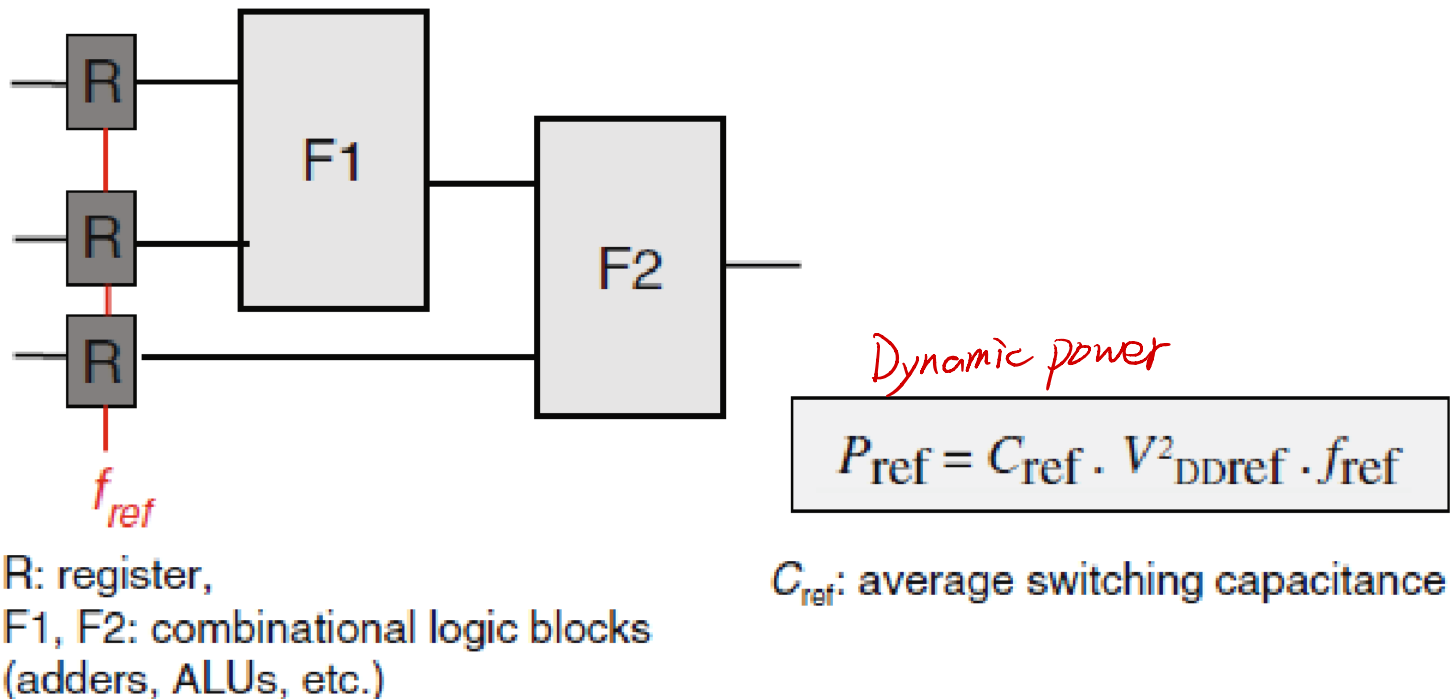

[A. Chandrakasan, JSSC'92]



Pipeline

 

$$f_{pipe} = f_{ref}$$

$$V_{DDpipe} = \varepsilon_{pipe} \cdot V_{DDref}$$


$$C_{pipe} = (1 + ov_{pipe}) \cdot C_{ref}$$

$$P_{pipe} = \varepsilon_{pipe}^2 \cdot (1 + ov_{pipe}) \cdot P_{ref}$$

Shallower logic reduces required supply voltage
(this example assumes equal V_{DD} for par / pipe designs)

Assuming $ov_{pipe} = 10\%$ $P_{pipe} = 0.66^2 \cdot 1.1 \cdot P_{ref} = 0.48 P_{ref}$

Parallel

 

$$f_{par} = f_{ref}/2$$

$$V_{DD\ par} = \epsilon_{par} \cdot V_{DD\ ref}$$

$$C_{par} = (2 + ov_{par}) \cdot C_{ref}$$

Almost cancels

$$P_{par} = \epsilon_{par}^2 \cdot \left(\frac{2 + ov_{par}}{2} \right) \cdot P_{ref}$$

Assuming
 $ov_{par} = 15\%$

$$P_{par} = 0.66^2 \cdot \frac{2.15}{2} \cdot P_{ref} = 0.47 P_{ref}$$

Outline

- Power Dissipation
 - Static Power Dissipation
 - Dynamic Power Dissipation
- Low Power Design Introduction
- Static Power Reduction
 - Multi Threshold Voltage
- **Dynamic Power Reduction**
 - Multi Voltage
 - Power Gating
 - RTL and Architecture Design Techniques
 - Clock gating
- Reference






Dynamic Clock Gating

➤ Why do we proceed clock gating

- Reduce the power consumption of registers by **turn off the un-used registers**
- Reduce the clock switching power

➤ Methods

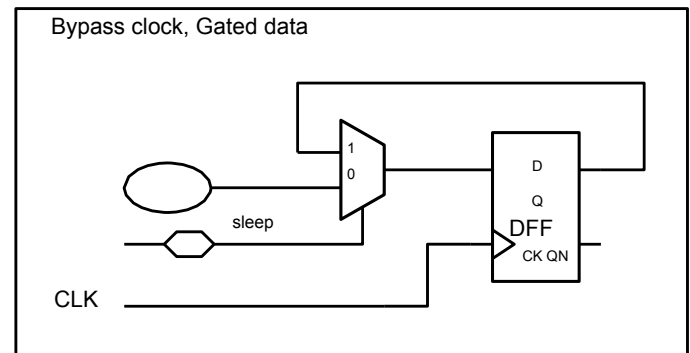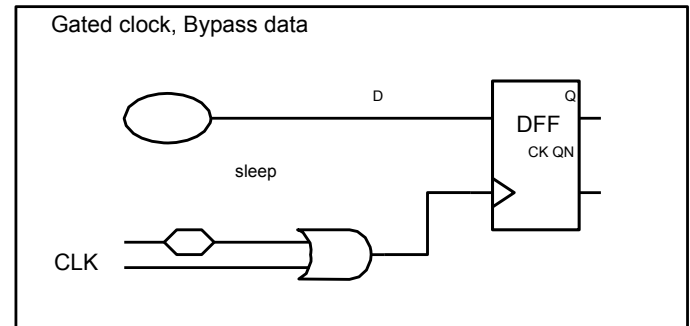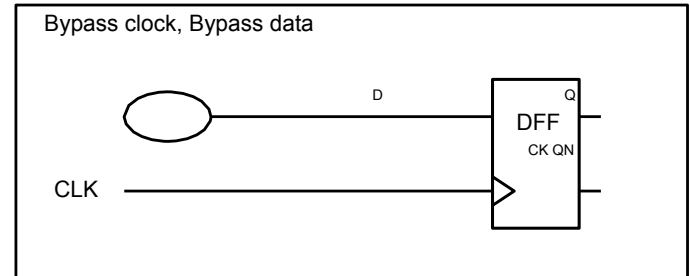- Gated clock, Bypass data.
- Bypass clock, Gated data.




Dynamic Clock Gating (cont.)

➤ Gated clock, bypass data

- For a design on ASIC, we do clock gating to reduce the power consumption.
- Notice that the gated condition should be chosen carefully

Gated clock, Bypass data

 

```
`ifdef SUPPORT_POWER_DOWN
    wire G_clock;
    wire G_sleep = ~( reset | ctrl1 | (~ctrl2) );
    GATED_OR GATED_G (
        .CLOCK( clock ),
        .SLEEP_CTRL( G_sleep ), // gated clock
        .CLOCK_GATED( G_clock )
    );
`else
    wire G_clock = clock;
`endif


always@(posedge G_clock) begin
    // bypass data
    if (reset) begin
        ..... end
    end else if (ctrl1) begin
        ..... end
    end else if (~ctrl2) begin
        ..... end
end
```

Dynamic Clock Gating (cont.)

➤ Gated clock, bypass data

- For a design on ASIC, we do clock gating to reduce the power consumption.
- Notice that the gated condition should be chosen carefully

Gated clock, Bypass data

 

```
`ifdef SUPPORT_POWER_DOWN
  wire G_clock;
  wire G_sleep = ~( reset | ctrl1 | (~ctrl2) );
  GATED_OR GATED_G (
    .CLOCK( clock ),
    .SLEEP_CTRL( G_sleep ), // gated clock
    .CLOCK_GATED( G_clock )
  );
`else
  wire G_clock = clock;
`endif

always@(posedge G_clock) begin
  // bypass data
  if (reset) begin
    ..... end
  end else if (ctrl1) begin
    ..... end
  end else if (~ctrl2) begin
    ..... end
end
```


判段是否全为0
G_sleep = 1
G_clock = 1
Clock gated !!
Gclock 不会有 posedge

Dynamic Clock Gating (cont.)

➤ Gated clock, bypass data

- For a design on ASIC, we do clock gating to reduce the power consumption.
- Notice that the gated condition should be chosen carefully

Gated clock, Bypass data

 

```
`ifdef SUPPORT_POWER_DOWN
    wire G_clock;
    wire G_sleep = ~( reset | ctrl1 | (~ctrl2) );
    GATED_OR GATED_G (
        .CLOCK( clock ),
        .SLEEP_CTRL( G_sleep ), // gated clock
        .CLOCK_GATED( G_clock )
    );
`else
    wire G_clock = clock;
`endif


always@(posedge G_clock) begin
    // bypass data
    if (reset) begin
        ..... end
    end else if (ctrl1) begin
        ..... end
    end else if (~ctrl2) begin
        ..... end
end
```

Annotations:
- **G_sleep = 0** (green)
- **G_clock = clock** (red)
- **Clock bypass !!** (blue, with arrow pointing to the **G_clock** signal in the always block)

Dynamic Clock Gating (cont.)

Bypass clock, Gated data

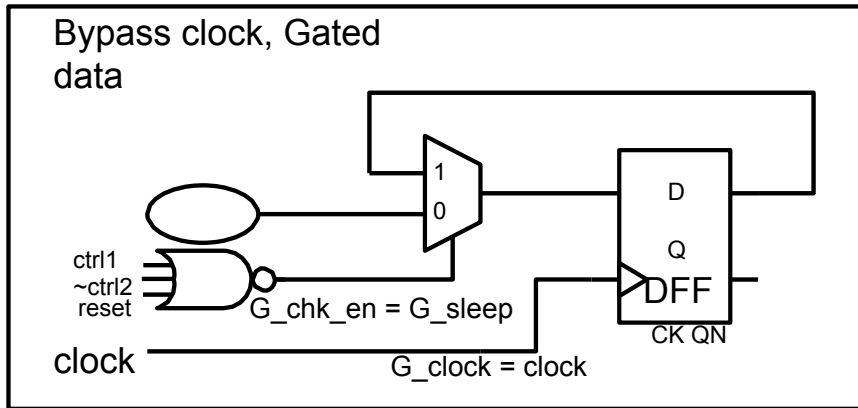- For a design on FPGA, the clock tree is pre-generated. **It is difficult to implement dynamic gated clock scheme.** Thus we do **data gating to minimize signal switching.**
- In order to logic equivalent with dynamic gated clock design, the data gating condition should be same with dynamic gated clock condition.



```

`ifdef SUPPORT_POWER_DOWN
    wire G_clock;
    wire G_sleep = ~( reset | ctrl1 | (~ctrl2)
    );
    wire G_chk_en = G_sleep;
    GATED_OR GATED_G (
        .CLOCK( clock ),
        .SLEEP_CTRL( 1'b0 ) // bypass clock
        .CLOCK_GATED(G_clock)
    );

```

↓
都先開

```
`else
    wire G_clock = clock;
`endif
```


```
always@(posedge G_clock) begin // gated data
    if ( !G_chk_en) begin
        if (reset) begin
            ..... end
        else if (ctrl1) begin
            ..... end
        else if (~ctrl2) begin
            ..... end
        end
    end
end
```



Dynamic Clock Gating (cont.)

➤ Bypass clock, Gated data

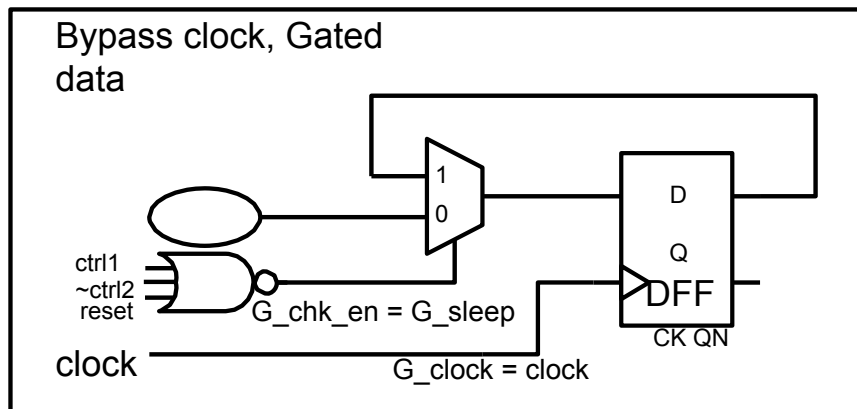- For a design on FPGA, the clock tree is pre-generated. **It is difficult to implement dynamic gated clock scheme.** Thus we do **data gating to minimize signal switching.**
- In order to logic equivalent with dynamic gated clock design, the data gating condition should be same with dynamic gated clock condition.



```

`ifdef SUPPORT_POWER_DOWN
    wire G_clock;
    wire G_sleep = ~( reset | ctrl1 | (~ctrl2) );
    wire G_chk_en = G_sleep;
    GATED_OR GATED_G (
        .CLOCK( clock ),
        .SLEEP_CTRL( 1'b0 ),
        bypass clock
        .CLOCK_GATED(G_clock)
    );
`else
    wire G_clock = clock;
`endif

always@(posedge G_clock) begin // gated data
    if ( !G_chk_en) begin
        if (reset) begin
            ..... end
        else if (ctrl1) begin
            ..... end
        else if (~ctrl2) begin
            ..... end
        end
    end
end
    
```


*G_sleep = 1
G_chk_en = 1
Data gated !!*

*再最外层
有因 G_chk_en*

Dynamic Clock Gating (cont.)

Bypass clock, Gated data

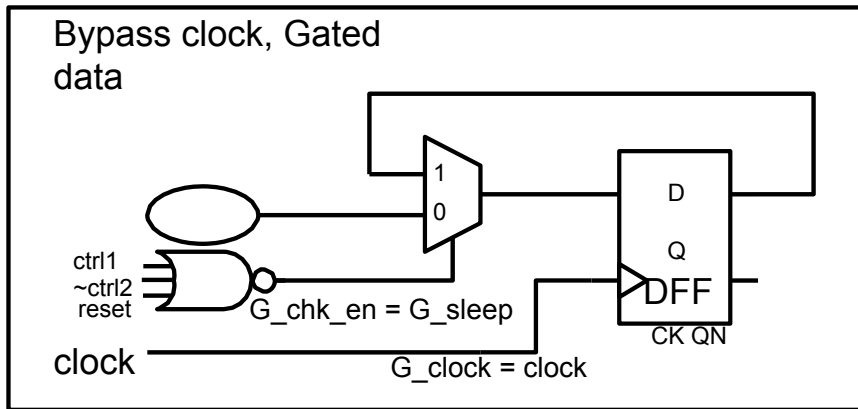- For a design on FPGA, the clock tree is pre-generated. **It is difficult to implement dynamic gated clock scheme.** Thus we do **data gating to minimize signal switching.**
- In order to logic equivalent with dynamic gated clock design, the data gating condition should be same with dynamic gated clock condition.



```


`ifdef SUPPORT_POWER_DOWN
    wire G_clock;
    wire G_sleep = ~( reset | ctrl1 | (~ctrl2)
    );
    wire G_chk_en = G_sleep;
    GATED_OR GATED_G (
        .CLOCK( clock ),
        .SLEEP_CTRL( 1'b0 ),           //
        bypass clock
        .CLOCK_GATED(G_clock)
    );
`else
    wire G_clock = clock;
    G_sleep = 0
    G_chk_en = 0
`endif
Data bypass !!

always@(posedge G_clock) begin // gated data
    if ( !G_chk_en) begin
        if (reset) begin
            ..... end
        else if (ctrl1) begin
            ..... end
        else if (~ctrl2) begin
            ..... end
        end
    end
end
end

```




Clock Gating Efficiently Reduces Power

 

90% of FFs clock-gated.

 70% power reduction by clock gating alone.





[Ref: M. Ohashi, ISSCC'02]

© IEEE 2002

Dynamic Clock Gating (cont.)

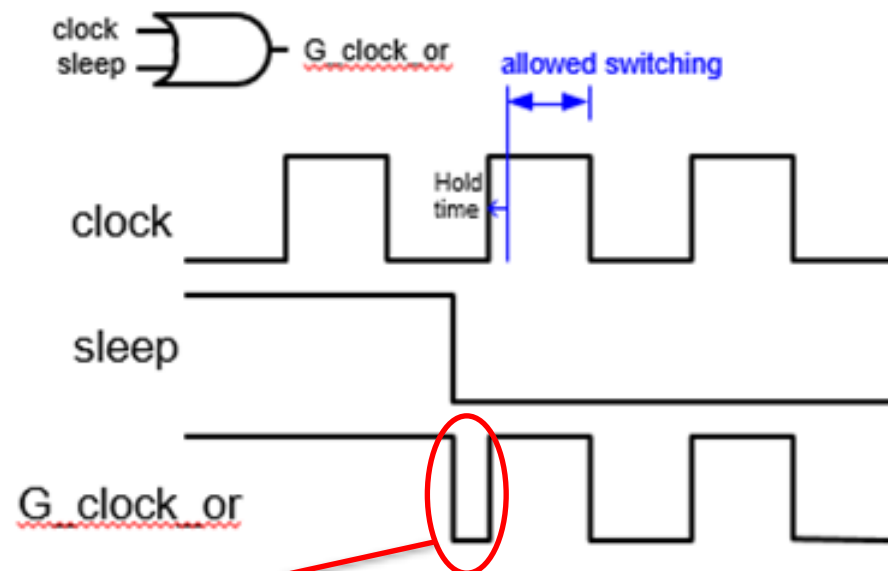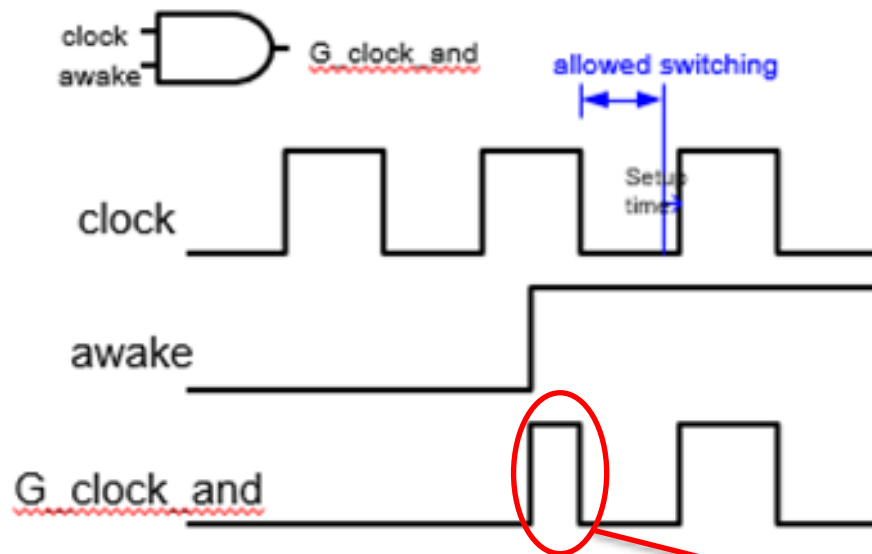- Clock gating can be implemented by **either AND-gating or OR-gating**
- The control signal can only change in specific half cycle
 - For clock rising edge trigger registers design
 - For AND gate, the allow switching cycle is clock at low period.
 - For OR gate, the allow switching cycle is clock at high period.





Timing issue!!







Dynamic Clock Gating (cont.)

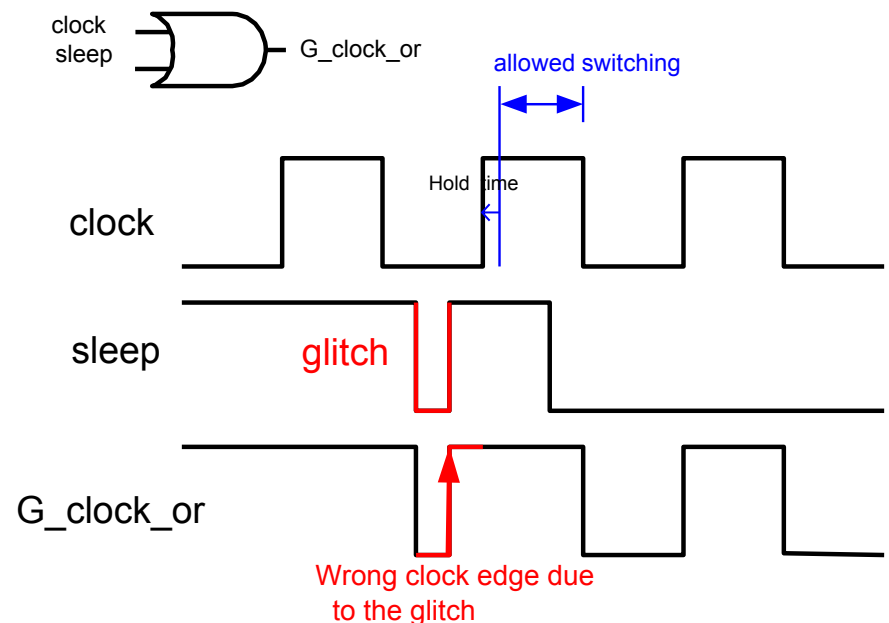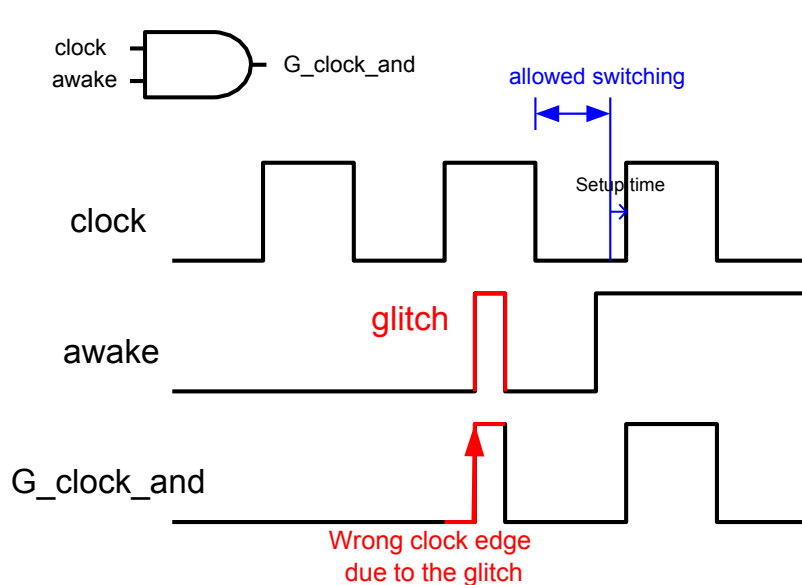- Clock gating can be implemented by either AND-gating or OR-gating
- The control signal can only change in specific half cycle
 - For clock rising edge trigger registers design
 - For AND gate, the allow switching cycle is clock at low period.
 - For OR gate, the allow switching cycle is clock at high period.





Dynamic Clock Gating (cont.)

➤ The method of avoid glitch

    

Dynamic Clock Gating (cont.)


➤ The method of avoid glitch

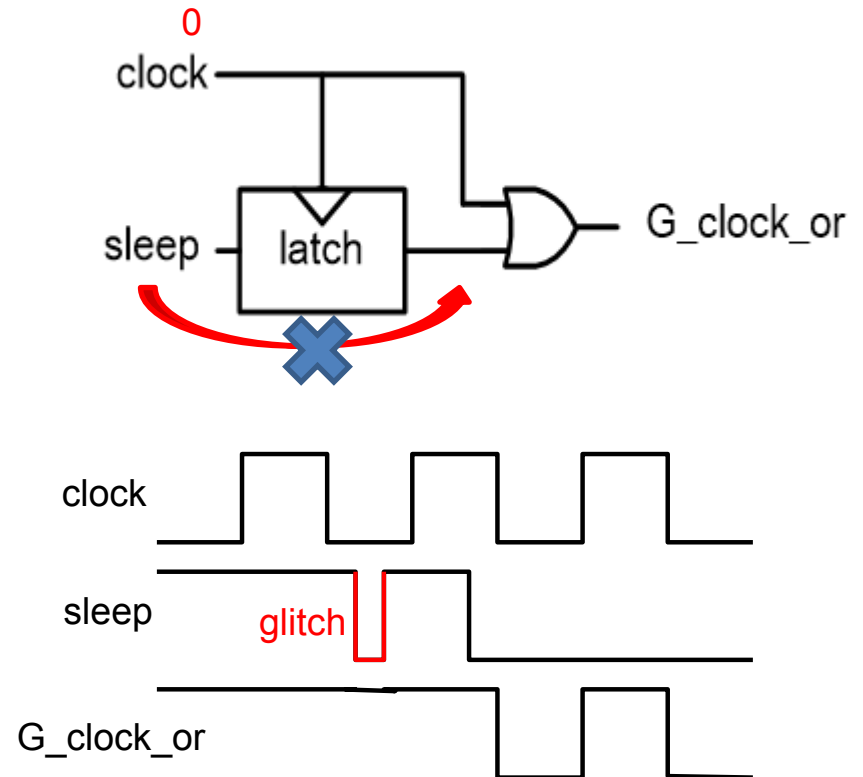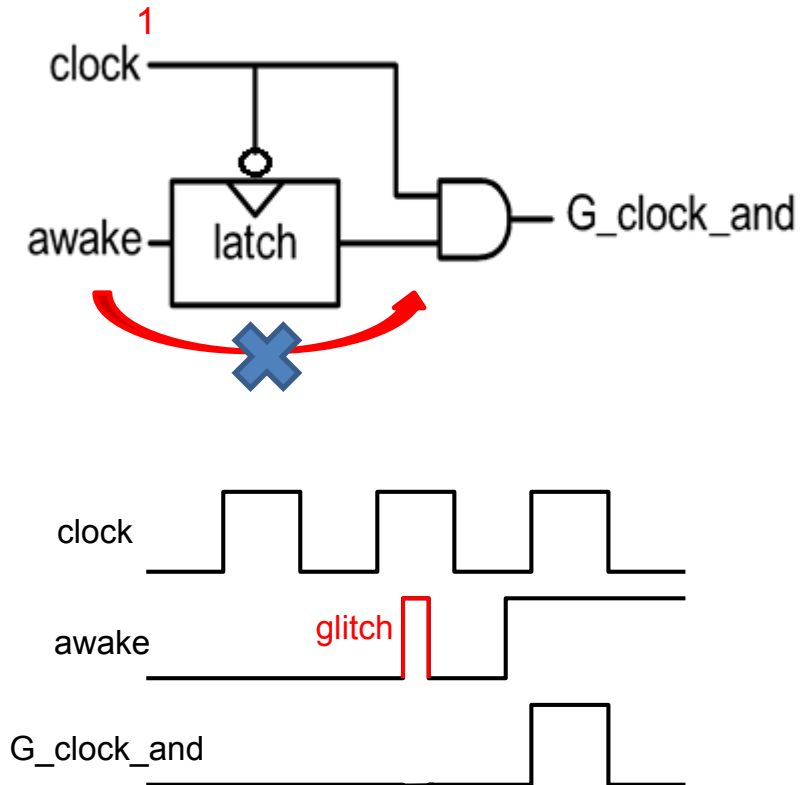

Dynamic Clock Gating (cont.)

➤ OR-gating is better


- **OR-gating consumes less power** than AND-gating
 - For OR-gating, the gated clock is tied at high when the register is turned off.
 - No matter data is toggling, the first latch circuits will not be toggled.
 - For AND-gating, the gated clock is tied at low when the register is turned off.
 - The **first latch circuits** will consume power as data input is switching.
- The gating control signals should be generated from clock rising edge
- flip-flops → stable gating the clock as clock high period
 - Consistent with original clock rising edge trigger registers design
 - It is easier for timing control and analysis

 

Dynamic Clock Gating (cont.)


➤ Notes

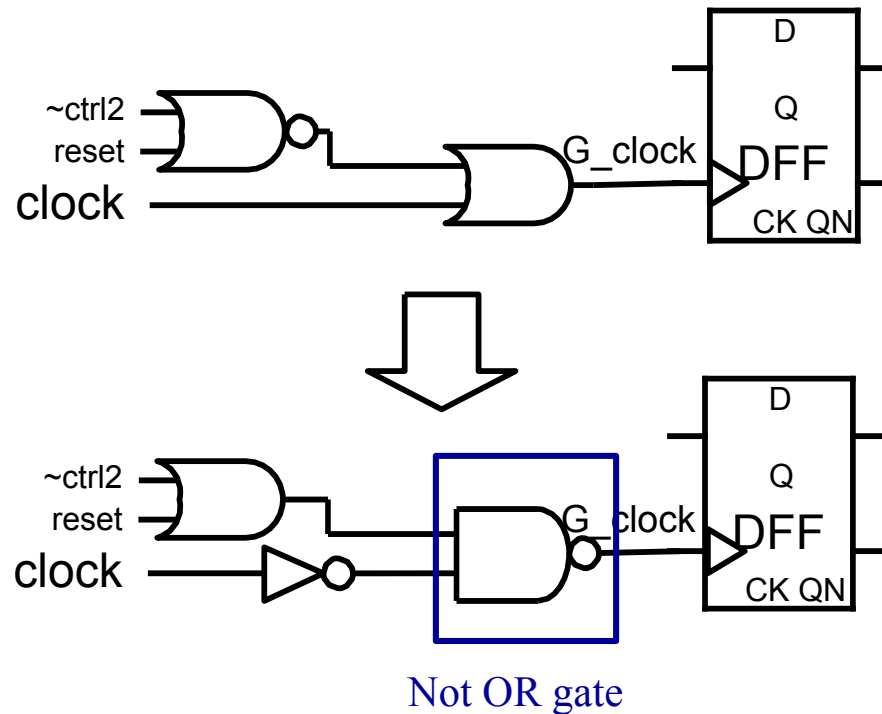- Writing OR gate in a single module can prevent the OR gate from being optimized with other logics during the synthesis




Clock Gating

- Power Saving

 

- Simpler skew management, less area.

 

- Keep the gates close to the registers. This allows for a fine-grain control on what to turn off and when. It comes at the expense of a more complex skew control and extra area.
- Move the gating devices higher up in the tree, which has the added advantage that the clock distribution network of the sub-tree is turned off. Modules cannot be turned off as often.

Reference

- Prof. S.J. Jou, “Low-Power Digital-IC”, The lecture note of DIC, 2014.
- S. S. Wang, “Logic Synthesis with Design Compiler”, The lecture of CIC course training, August 2008.
- M. Keating, D. Flynn, R. Aitken, A. Gibbons, K. shi, “Low Power Methodology Manual”.
- Arman Vassighi, Manoj Sachdev, “Thermal Runaway in Integrated Circuits” , June 2006.



Introduction to Power Simulation by Using **PrimeTime**

NCTU-EE ICLab Spring-2022



Lecturer : Yu Lin, Hsu

Outline


- **Start PrimeTime**
- **Simulation Flow of PrimeTime**
 - Phase 1 -- relative file preparation
 - Phase 2 -- power analysis
- **Reports Analysis**
- **A Power Analysis Script Example**



Start PrimeTime

- Interfaces of PrimeTime
 - Command-line interface
 - **pt_shell**
 - Graphical user interface
 - **pt_shell -gui**

pt_shell>

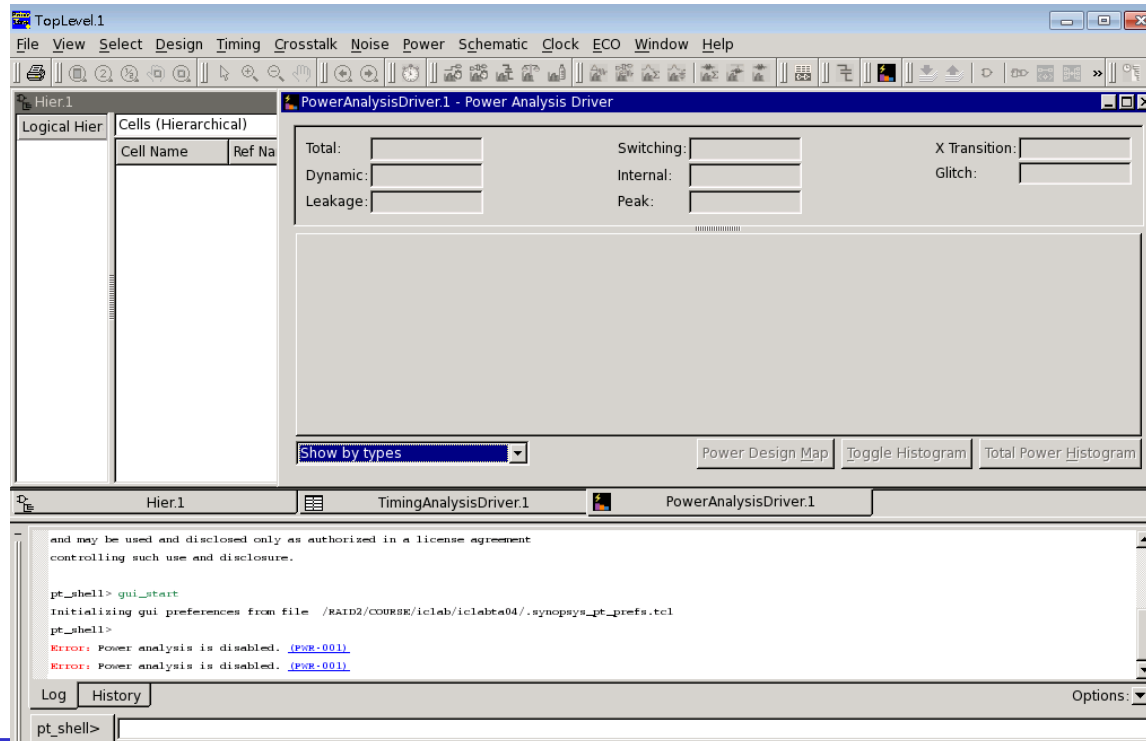

Start PrimeTime (cont.)


- PrimeTime supports command in tcl mode
 - Tcl : tool command language (tcl) has a straightforward syntax.
- Start using PrimeTime
 - Start pt_shell (the PrimeTime command-line interface)
 - Command : `pt_shell`
 - Start PrimeTime graphical user interface (GUI)
 - Command : `pt_shell -gui`
 - Run scripts in pt_shell gui
 - Command : `source filename.tcl`
 - Get command help
 - Command : `man command_name`
 - Exit PrimeTime
 - Command : `exit`



Simulation Flow


Value Change Dump

VCD Flow

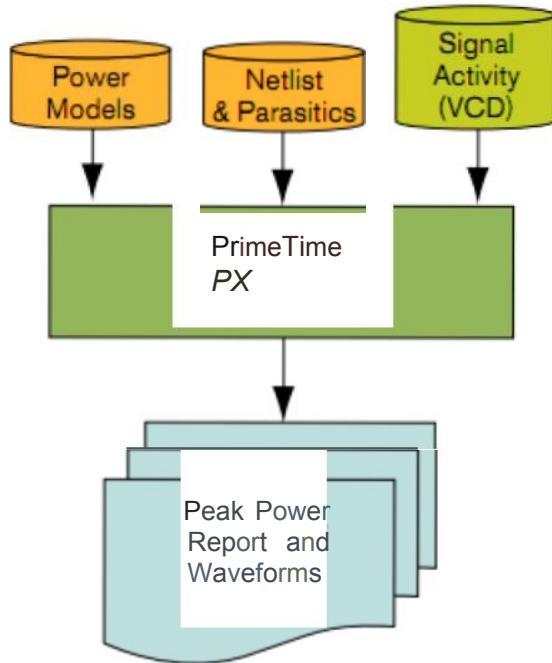

Switching Activity Interchange Format

SAIF Flow

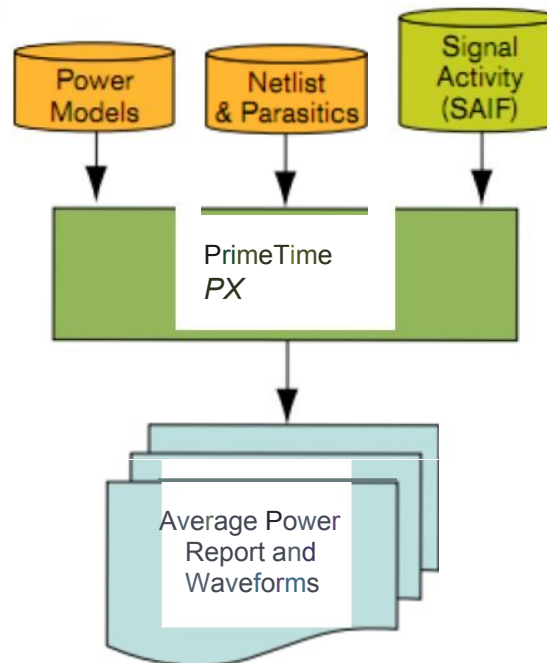

Vector-free Flow

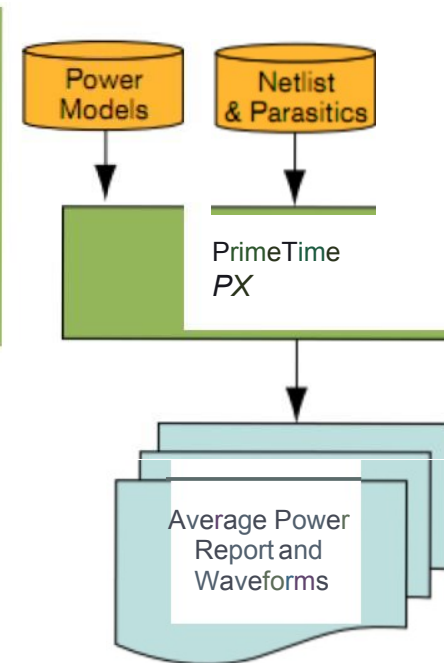


Figure 4: Power Analysis Flows.

VCD file : Contains value changes of a signal.
i.e. at what times signals changes their values.

SAIF file : contains toggle counts and time information like how much time a signal was in 1 state, 0 state , x state.

It contains cumulative information of vcd.

Simulation Flow (cont.)

- PrimeTime's simulation flow contains two phases
 - Phase 1 -- relative file preparation
 - Technology library
 - Gate-level netlist
 - Switching activity file (Value Change Dump file or FSDB file)
 - Synopsys design constraint (SDC file)
 - Standard delay format (SDF file)
 - Parasitic file (after APR) (RSPF, SPEF, or DSPF file)
 - Phase 2 -- power analysis
 - Specify search path and link libraries
 - Read design and link design
 - Read switching activity file
 - Set transition time and annotate parasitics
 - Generate power report



Simulation Flow : Phase 1

➤ Phase 1 -- related files preparation

— Technology library

- The file contains library cells, which has timing, power and characterization information.
- Internal and leakage power are in the library
- The library used for power analysis should be the same with the library used for synthesis
- The technology libraries are provided by foundry, and are specified in the startup file.



Simulation Flow : Phase 2

➤ Phase 2 -- power analysis

— Specify search path

- Search path is a list of directories for PrimeTime to read design and library files
- Command : `set search_path { absolute_path or relative_path }`
 - ◆ Example : `set search_path { ./library ./source_code }`

— Specify link library

- The link_library variable specifies where and in what order PrimeTime looks for design files and library files for linking the design
- Command: `set link_library { * library_name }`
 - ◆ Use an asterisk (*) to make PrimeTime search for designs in memory
 - ◆ Example : `set link_library { * slow.db }`



Simulation Flow : Phase 2 (cont.)

— Read design

- The design for power analysis must be a structural, fully mapped gate-level netlist.
- The netlist cannot contain any high-level constructs
- Command : `read_verilog file_names`
 - ◆ Example : `read_verilog CHIP.v`

— Set current design

- Before link design, specify the current design first
- Command : `current_design design_name`
 - ◆ Example : `current_design YOUR_DESIGN`

— Link design

- Resolve references in a design
- Command : `link_design [design_name]`
 - ◆ `design_name` : specify design name to be linked. (Default is current design)
 - ◆ Example : `link_design`



Simulation Flow : Phase 2 (cont.)

— Read switching activity file

- The switching activity information used for power calculation is in the VCD or FSDB format generated and dumped out from the simulation
- Command : `read_vcd [-strip_path strip] file_name`
 - ◆ `[-strip_path strip]` : specifies a path prefix that is to be stripped from all the object names read from the VCD file or FSDB file
 - ◆ **PrimeTime will transform FSDB file into VCD file automatically**
 - ◆ Example : if the VCD or FSDB file is generated from module TESTBED and the instance name of the design is I_YOUR_DESIGN
→ `read_vcd -strip_path TESTBED/I_YOUR_DESIGN CHIP.vcd`

— Read design constraint file

- It is unnecessary to re-specify design constraints. Designer can simply include the SDC file generated during synthesis
- Command : `read_sdc [-syntax_only] file_name`
 - ◆ `[-syntax_only]` : only process the syntax check of SDC file
 - ◆ Example : `read_sdc CHIP.sdc`



Simulation Flow : Phase 2 (cont.)

— Annotate delay information

- Designer can include the delay information generated during synthesis
- Command: `read_sdf [-load_delay net | cell] [-syntax_only] file_name`
 - ◆ `[-load_delay net | cell]` : indicate whether load delays are included in net delays or in cell delays
 - ◆ `[-syntax_only]` : only process the syntax check of SDC file
 - ◆ Example : `read_sdf -load_delay net CHIP.sdf`

— Set transition time

- PrimeTime uses the transition time defined at each input port to calculate the cell power consumption and transition times for the following logic stages
- Command : `set_input_transition transition_time port_list`
 - ◆ Example : `set_input_transition 0.1 [all_inputs]`



Simulation Flow : Phase 2 (cont.)

– Generate power waveforms

- To save the power values over time, designer can make PrimeTime stores the power for every event within a given time interval in a waveform file.
- Command : `set_power_analysis_options -waveform_interval [-format fsdb | out] [-file file_prefix]`
 - ◆ `waveform_interval` : specify the sampling interval for power calculation (unit : ns)
 - ◆ `[-file file_prefix]` : set the prefix for the output files (default : PrimeTime)
 - ◆ `[-format fsdb | out]` : specify the waveform format
 - » `fsdb` : PrimeTime default value, can be viewed by nWave
 - » `out` : PrimeTime will output a text .out file
 - » `rpt` : PrimeTime does not output waveform, but display peak power in .rpt file
 - ◆ Example : `set_power_analysis_options -waveform_interval 1 -waveform_format out -waveform_output vcd`


Will create file “vcd.out”



Simulation Flow : Phase 2 (cont.)

– Generate power waveforms

- To save the power values over time, designer can make PrimeTime stores the power for every event within a given time interval in a waveform file.
- Command : `set_power_analysis_options -waveform_interval [-file file_prefix] [-format fsdb | out]`
 - ◆ -waveform_output fsdb example

 

Simulation Flow : Phase 2 (cont.)

— Generate default power reports

- PrimeTime can generate a wide range of reports that provide information about the power consumption
- Command : `report_power [-file file_prefix] [-leaf] [-nosplit] [-sortby [power | toggle | name]]`
 - ◆ `[-leaf]` : reports power for leaf instances
 - ◆ `[-sortby [power | toggle | name]]` : sort the instances in the .rpt file
 - » Power : sort by power values
 - » Toggle : sort by toggle counts
 - » Name : sort by name
 - ◆ `[-nosplit]` : to prevent line-splitting or section-breaking
 - ◆ Example : `report_power -file CHIP -sortby power -leaf`



Reports Analysis

✓ Default power report analysis

Power Group	Internal Power	Switching Power	Leakage Power	Total Power	(%)	Attrs
clock_network	0.0000	0.0000	0.0000	0.0000	(0.00%)	
register	2.213e-03	4.254e-05	1.126e-06	2.257e-03	(81.94%)	i
combinational	3.232e-04	1.713e-04	2.802e-06	4.973e-04	(18.06%)	
sequential	0.0000	0.0000	0.0000	0.0000	(0.00%)	
memory	0.0000	0.0000	0.0000	0.0000	(0.00%)	
io_pad	0.0000	0.0000	0.0000	0.0000	(0.00%)	
black_box	0.0000	0.0000	0.0000	0.0000	(0.00%)	


Net Switching Power	=	2.139e-04	(7.77%)			
Cell Internal Power	=	2.536e-03	(92.09%)			
Cell Leakage Power	=	3.928e-06	(0.14%)			
Intrinsic Leakage	=	3.928e-06				
Gate Leakage	=	0.0000				

Total Power	=	2.754e-03	(100.00%)			
X Transition Power	=	2.613e-06				
Glitching Power	=	0.0000				
Peak Power	=	0.0247				
Peak Time	=	114120				



Appendix A

 Dynamic Clock Gating For Different Syntheses



Dynamic Clock Gating (cont.)

✓ A general design Verilog coding

- For ASIC synthesis
 - `define FPGA_SYN 0
 - Bypass data, gated clock
- For FPGA synthesis
 - `define FPGA_SYN 1
 - Gated data, bypass clk

```
`ifndef SUPPORT_POWER_DOWN
    wire G_clock;
    wire G_sleep = ~( reset | ctrl1 | (~ctrl2) );
    wire G_gated = G_sleep & ~( `FPGA_SYN
    );
    wire G_chk_en = ( `FPGA_SYN == 0 )? 1'b0 :
    G_sleep;
    GATED_OR GATED_G (
        .CLOCK( clock ),
        .SLEEP_CTRL( G_gated ),
        .CLOCK_GATED( G_clock )
    );
`else
    wire G_clock = clock;
    wire G_chk_en = 0;
`endif

always@(posedge G_clock)
begin
    if ( !G_chk_en)
    begin
        if (reset)
        begin
            ..... end
        else if (ctrl1)
        begin
            ..... end
        else if (~ctrl2)
        begin
            ..... end
        end
    end end
```



Dynamic Clock Gating (cont.)

✓ A general design Verilog coding

- For ASIC synthesis
 - `define FPGA_SYN 0
 - Bypass data, gated clock
- For FPGA synthesis
 - `define FPGA_SYN 1
 - Gated data, bypass clk

```
`ifndef SUPPORT_POWER_DOWN
    wire G_clock;
    wire G_sleep = ~( reset | ctrl1 | (~ctrl2) );
    wire G_gated = G_sleep & ~( `FPGA_SYN );
    wire G_chk_en = ( `FPGA_SYN == 0 )? 1'b0 : G_sleep;
    GATED_OR GATED_G (
        .CLOCK( clock ),
        .SLEEP_CTRL( G_gated ),
        .CLOCK_GATED( G_clock )
    );
`else
    wire G_clock = clock;
    wire G_chk_en = 0;
`endif

always@(posedge G_clock)
begin
    if ( !G_chk_en )
    begin
        if (reset)
        begin
            ..... end
        else if (ctrl1)
        begin
            ..... end
        else if (~ctrl2)
        begin
            ..... end
        end end
end end
```

FPGA_SYN = 0
G_chk_en = 0
Data bypass !!



Dynamic Clock Gating (cont.)

✓ A general design Verilog coding

- For ASIC synthesis
 - `define FPGA_SYN 0
 - Bypass data, gated clock
- For FPGA synthesis
 - `define FPGA_SYN 1
 - Gated data, bypass clk

```
`ifdef SUPPORT_POWER_DOWN
    wire G_clock;
    wire G_sleep = ~( reset | ctrl1 | (~ctrl2) );
    wire G_gated = G_sleep & ~( `FPGA_SYN );
    wire G_chk_en = ( `FPGA_SYN == 0 )? 1'b0 : G_sleep;
    GATED_OR GATED_G (
        .CLOCK( clock ),
        .SLEEP_CTRL( G_gated ),
        .CLOCK_GATED( G_clock )
    );
`else
    wire G_clock = clock;
    wire G_chk_en = 0;
`endif

always@(posedge G_clock)
begin
    if ( !G_chk_en )
    begin
        if (reset)
        begin
            ..... end
        else if (ctrl1)
        begin
            ..... end
        else if (~ctrl2)
        begin
            ..... end
        end end
end end
```

FPGA_SYN = 0
G_chk_en = 0
Data bypass !!
G_gated = G_sleep
If G_sleep = 1
G_clock = 1
Clock gated !!



Revision History

- 2007 Kuan-Ling Kuo (amos@si2lab.org)
- 2008 Yao-Lin Chen (arrayz@si2lab.org)
- 2013 Yu-Tao Yang (futurestar@si2lab.org)
Rong-Jie Liu (johnny510.ee98@g2.nctu.edu.tw)
- 2014 Hsin_Yi Yu (cindy19212002@gmail.com)
- 2015 Sheng Wan (vjod@si2lab.org)
Renxuan Yu (yurx1123@gmail.com)
- 2017 Tsu-Jui Hsu (johnson711309@gmail.com)
- 2018 Po-Yu Huang (hpv35269@gmail.com)
Chien-Hao Chen (coreldraw8083@gmail.com)
- 2019 Chi-Yuan Sung (sam850325@gmail.com)
- 2020 Cheng-Han Huang (huang50216@gmail.com)
- 2021 Shao-Wen Cheng (shaowen0213@gmail.com)
- 2022 Yu-Lun Hsu (hdy986@gmail.com)

